

# 1. Finite State Machines (FSMs)

- **Definition:** A model with a finite number of states, transitions triggered by inputs.
- **Used for:** Modeling behavior where the *order of inputs matters* (e.g. string recognition, coin counters, locker combos).
- **Examples:**
  - Detect strings ending in 'a' or 'b'.
  - Accept \$5 in \$1/\$2 coins.
  - Bit sequences ending in 1 but excluding 00.
  - 1-bit storage using FSM logic.

# 2. FSMs to Circuits

- **Feedback loops** in FSMs = sequential circuits.
- **Sequential Logic:** Stores information over time using feedback (Q feeds back into logic).
- **Problems without refresh:** Signal degrades due to noise/attenuation.
- **Solution:** Use NOT gates for basic refresh or introduce memory elements (like flip-flops).

# 3. Oscillators and Clock

- **Oscillators:** Circuits that toggle between 0 and 1 based on propagation delay.
- **Clock:** Synchronizes operations in CPU (load → compute → store).
- **Clock Edge Timing:**
  - Positive edge: triggers load or add.
  - Negative edge: triggers store.

---

## 4. Latches and Flip-Flops

### Latches

- **S-R Latch:** Basic 1-bit memory.
  - S (Set) → stores 1.
  - R (Reset) → stores 0.
  - Simultaneous S=R=1 is undefined.

### Flip-Flops

- **SR Flip-Flop:** Clocked version of S-R latch (edge-triggered).
- **JK Flip-Flop:** J=K=1 toggles output.
- **D Flip-Flop:** Simplified (D=1 sets to 1, D=0 sets to 0).

## 5. Registers

- **Definition:** Small, fast storage used directly by CPU.
- **Types:**
  - Program Counter (PC)
  - Memory Address Register (MAR)
  - Memory Buffer Register (MBR)
  - Status Register (flags)
  - General Purpose Registers
- **Loading:**

- **Serial:** Bit-by-bit input.
- **Parallel:** Whole word input (faster).

## 6. Counters

- Specialized registers that increment automatically.
- Used in program counters and loops.

## 7. Types of Memory

Type	Volatility	Density	Cost	Use
<b>Magnetic</b>	Permanent	High	Low	HDD
<b>Flash</b>	Permanent	High	Low	SSD
<b>Capacitors</b>	Volatile	Medium	Medium	DRAM (main memory)
<b>Flip-Flops</b>	Volatile	Low	High	SRAM (cache)