

### Karnaugh map

\* Circle cells so that the bits never flip stay, and the bits that flip disappear. \*

- Lay rows/columns in gray code order (00, 01, 11, 10)
- Group 1's for sum of products
- Group 0's for product of sums
- Make every group a power of 2

|   |   | AB |    |    |    |    |
|---|---|----|----|----|----|----|
|   |   | C  | 00 | 01 | 11 | 10 |
| A | B | 0  | 0  | 1  | 1  | 0  |
|   |   | 1  | 0  | 0  | 0  | 1  |

What changes?

→ Mission for group 1: When C is always 0, B stays the same but A changes. Therefore, the outputs for the 2 1's do not depend on A.  
depends on B  
\* look for variable that doesn't change

$B\bar{C}$

since the output is 1 when C is 0, we put not C ( $\bar{C}$ )

→ for group 2, C changes. It is independent of C. AB is same.  
A is 1, matches output, but B is 0 so  $\bar{B}$

$$F = BC' + AB$$


$$= 1(1) + 0(1)$$

$$= 1(0) + 0(0) = 0V$$

match output

$$F = BC' + AB = \textcircled{BC'} \oplus \textcircled{AB}$$

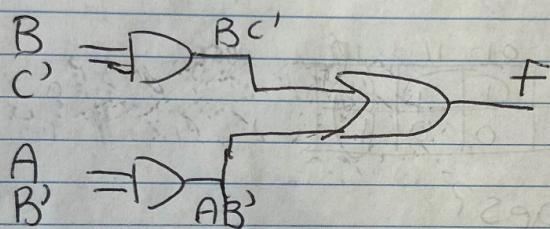Need an AND gate to connect ~~BC'~~  
and  $AB$



Manu

Example 2:

Group 3: AMBABC'

|  |  | A | BC | 0 | 1 |
|--|--|---|----|---|---|
|  |  | 0 | 0  | 0 | 1 |
|  |  | 1 | 0  | 1 | 1 |
|  |  | 1 | 1  | 1 | 0 |
|  |  | 0 | 0  | 0 | 0 |

Group 2: A always 0,  
C always 1, B changes

$$A'C + B$$

Group 1: B never changes, A is always 1,  
but C changes, so dependent on C

$$B' A B'$$

## Simplifying Algebra Equations

① Expression:  $Y = A \cdot A + A \cdot B$

→ Since  $A \cdot A = A$

M

$$Y = A + A \cdot B$$

Absorption law:  $A + A \cdot B = A$

②  $y = A \cdot (A + B)$  so  $y = A$

Absorption law  $\rightarrow A + B = A$

$$A \cdot A = A \rightarrow Y = A$$

③  $y = A + \bar{A} + B$

$A \cdot \bar{A} = 0$  (inverse)

$0 + B = B$  (identity)

Y = B

④  $y = (A + B)(A + \bar{B})$

distributive:  $(A + B)(A + \bar{B}) = A + (B \cdot \bar{B})$

Inversc:  $B \cdot \bar{B} = 0$

$$A + 0 = A$$

Y = A

⑤  $\bar{A} + \bar{B}$

demorgan:  $\bar{A} \cdot \bar{B}$

⑥  $y = \bar{A} \cdot \bar{B} + A$

demorgan:  $\bar{A} + \bar{B} + A$

$$\bar{A} + A = 1$$

$$1 + \bar{B} = 1$$

Y = 1